

# MONOSTABLE MULTIVIBRATORS

## SUMMARY

- A monostable multivibrator has one stable state and one quasi-stable state.
- The main application of a monostable multivibrator is as a gate that generates a pulsed output.
- The gate width of collector-coupled monostable multivibrator is liable to change with temperature variations.
- A monostable multivibrator can be used as a voltage-to-time converter.
- In a collector-coupled monostable multivibrator, to ensure that the gate width remains constant, the ON device is required to be driven into saturation, in the quasi-stable state.
- The emitter-coupled monostable multivibrator may operate as a free-running multivibrator if  $V > V_{(\max)}$ .
- In an emitter-coupled monostable multivibrator, even if the ON device is held in the active region; in the quasi-stable state, because of a substantial emitter-resistance which stabilizes the current, the gate width can be maintained stable.

## MULTIPLE CHOICE QUESTIONS

1. A monostable multivibrator is also known by the name:
  - a) Flip-flop
  - b) Free-running multivibrator
  - c) One-shot multivibrator
  - d) Schmitt trigger
2. A monostable multivibrator can be used as a:
  - a) Voltage-to-time converter
  - b) Clock
  - c) Squaring circuit
  - d) Flip-flop
3. The gate width of a collector-coupled monostable multivibrator in which the ON device, in the quasi-stable state, is in saturation is given by the relation:
  - a)  $T = 0.69 RC$
  - b)  $T = 69 RC$
  - c)  $T = \sqrt{0.69RC}$
  - d)  $T = \sqrt{69RC}$
4. The multivibrator that can be used as a gating circuit is:
  - a) Bistable multivibrator
  - b) Schmitt trigger
  - c) Monostable multivibrator
  - d) Astable multivibrator
5. The gate width of an emitter-coupled multivibrator is:
  - a) Independent of temperature variation
  - b) Varies with temperature
  - c) Varies with variation of device parameters
  - d) None of the above

6. The expression for the gate width of collector-coupled monostable multivibrator, considering  $I_{CO}$  is given by:

- a)  $T = 0.69RC$
- b)  $T = \sqrt{0.69RC}$
- c)  $T = 69RC$
- d)  $T = \tau \ln 2 - \tau \ln [(1 + \phi)/(1 + \phi/2)]$

### SHORT ANSWER QUESTIONS

1. The main application of a monostable multivibrator is as a gating circuit, explain.
2. Explain, how you can use a monostable multivibrator as a voltage-to-time converter.
3. The expression for the gate width of a collector-coupled monostable multivibrator is given as  $T = \tau \ln (V_{CC} - V_{\sigma} + I_1 R_C) / (V_{CC} - V_T)$  where  $I_1$  is the current in  $Q_1$ , when ON in the quasi-stable state. If the ON device is driven into saturation, show that  $T = 0.69\tau$ .
4. What is the main advantage of an emitter-coupled monostable multivibrator over collector-coupled monostable multivibrator?
5. Draw the circuit of an emitter-coupled monostable multivibrator and explain its operation.

### LONG ANSWER QUESTIONS

1. Draw the circuit of a collector-coupled monostable multivibrator and explain its operation. Obtain the expression for its gate width and show that the gate width can be stable if the ON device is driven into saturation, in the quasi-stable state. Draw the waveforms.
2. Draw the circuit of a voltage-to-time converter and obtain the expression for the time period.
3. With the help of a circuit diagram and waveforms, explain the working of an emitter-coupled monostable multivibrator. Derive the expression for its gate width.

### SOLVED PROBLEMS

**Example 8.1:** Calculate the gate width for the monostable multivibrator given that  $R = 100 \text{ k}\Omega$ ,  $V_{CC} = 10 \text{ V}$ ,  $C = 0.01 \text{ }\mu\text{F}$ ;

**Solution:**

$$\tau = RC = 100 \times 10^3 \times 0.01 \times 10^{-6} = 1 \text{ ms}$$

$$T = 0.69 \times 100 \times 10^3 \times 0.01 \times 10^{-6} = 0.69 \text{ ms.}$$

**Example 8.6:** For the monostable multivibrator shown in Fig. 8.1,  $R_1 = R_2 = R = 20 \text{ k}\Omega$ ,  $C = 0.01 \text{ }\mu\text{F}$ ,  $R_C = 2 \text{ k}\Omega$ ,  $V_{CC} = 12 \text{ V}$ ,  $V_{BB} = -12 \text{ V}$ . Find the time period  $T$ .

**Solution:**

$$\text{Time period } T = 0.69RC = 0.69 \times 20 \times 10^3 \times 0.01 \times 10^{-6} = 138 \text{ }\mu\text{s}$$

**Example 8.2:** Consider the circuit shown in Fig. 8.8(a), which uses an  $n-p-n$  silicon transistors with the following specifications:  $V_{CC} = 10\text{ V}$ ,  $V_{BB} = 10\text{ V}$ ,  $R_C = 1\text{ k}\Omega$ ,  $R_1 = 10\text{ k}\Omega = R$ ,  $R_2 = 100\text{ k}\Omega$ ,  $h_{FE(\min)} = 30$ ,  $r_{bb} = 0.2\text{ k}\Omega$ ,  $V_{CE(\text{sat})} = 0.3\text{ V}$ ,  $V_{BE(\text{sat})} = V_{\sigma} = 0.7\text{ V}$ . Calculate all the current and voltages and then plot the waveforms.

**Solution:** (i) In the stable state ( $t < 0$ )

The assumption made is  $Q_2$  is ON and in saturation and  $Q_1$  is OFF. To verify that  $Q_2$  is ON and in saturation,  $I_{C2}$  and  $I_{B2}$  of  $Q_2$  are to be calculated. Further check whether  $I_{B2} \gg I_{B2}(\min)$  or not. If  $I_{B2} \gg I_{B2}(\min)$ , then  $Q_2$  is really in saturation. Consider the circuit shown in Fig. 8.8(b).

(a) To verify if  $Q_2$  is ON and in saturation:

$$I_{C2} = I_2 - I_3 \quad I_2 = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C} = \frac{10 - 0.3}{1\text{ k}\Omega} = 9.7\text{ mA}$$

$$I_3 = \frac{V_{CE(\text{sat})} - (-V_{BB})}{R_1 + R_2} = \frac{10.3}{110\text{ k}\Omega} = 0.0934\text{ mA}$$

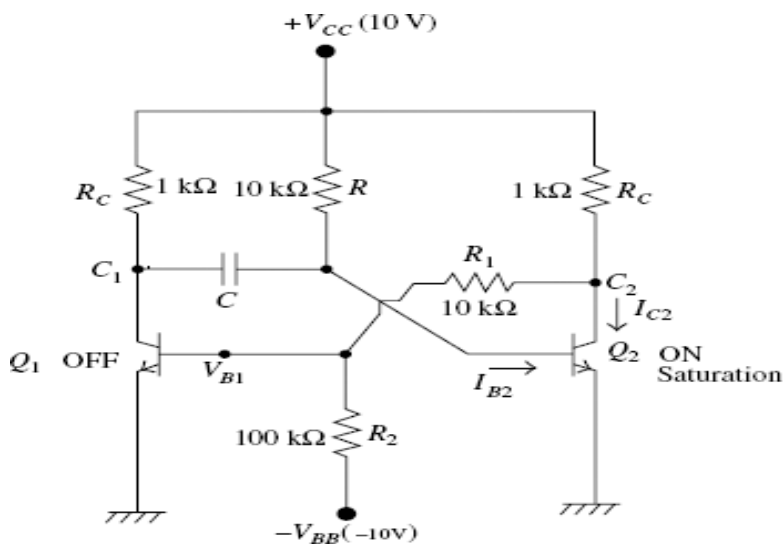


FIGURE 8.8(a) Practical collector-coupled monostable multivibrator

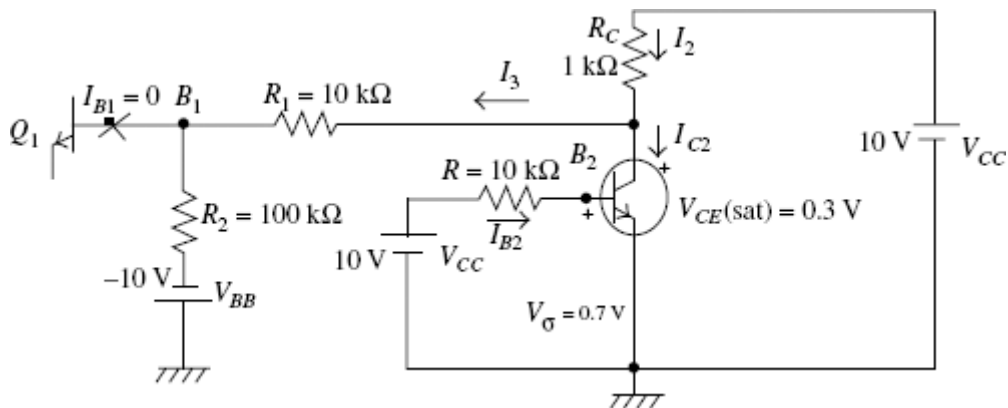


FIGURE 8.8(b) In the stable state,  $Q_1$  is OFF and  $Q_2$  is ON

$$\therefore I_{C2} = I_2 - I_3 = 9.7 \text{ mA} - 0.0934 \text{ mA} = 9.61 \text{ mA}$$

$$I_{B2} = \frac{V_{CC} - V_{\sigma}}{R} = \frac{10 - 0.7}{10 \text{ k}\Omega} = 0.93 \text{ mA} \quad I_{B2(\text{min})} = \frac{I_{C2}}{h_{FE(\text{min})}} = \frac{9.61 \text{ mA}}{30} = 0.32 \text{ mA}$$

For  $Q_2$  to be in saturation,  $I_{B2}$  should be at least  $1.5 I_{B2(\text{min})}$ . Hence,  $I_{B2}$  should be selected to keep  $Q_2$  in saturation as

$$I_{B2} = 1.5 \times 0.32 \text{ mA} = 0.48 \text{ mA}.$$

As  $I_{B2}(0.93 \text{ mA}) \gg 1.5 I_{B2(\text{min})}(0.48 \text{ mA})$ , as per the assumption made  $Q_2$  is really in saturation. Hence,

$$V_{C2} = 0.3 \text{ V, and } V_{B2} = 0.7 \text{ V}.$$

b) To verify that  $Q_1$  is OFF:

To verify whether  $Q_1$  is in the OFF state or not,  $V_{B1} = V_{BE1}$  is calculated and seen if it reverse-biases the base-emitter diode. The voltage  $V_{B1}$  is due to two sources—the  $V_{BB}$  source and the  $V_{CE(\text{sat})}$  source, as shown in Fig. 8.8(c). Use the superposition theorem to calculate  $V_{B1}$ , considering one source at a time. Considering the  $V_{CE(\text{sat})}$  source and shorting the  $V_{BB}$  source, the resultant circuit is as shown in Fig. 8.8(d).

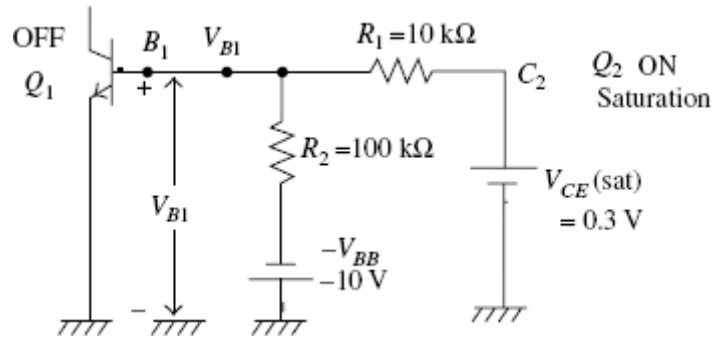


FIGURE 8.8(c) The circuit for calculating  $V_{B1}$

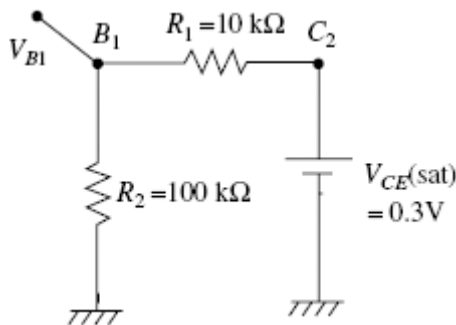


FIGURE 8.8(d) The circuit to calculate  $V_{B1}$  due to  $V_{CE(\text{sat})}$  source

$$V_{B1}(V_{BB} = 0) = V_{CE(\text{sat})} \times \frac{R_2}{R_1 + R_2} = 0.3 \times \frac{100}{100 + 10} = \frac{3}{11} = 0.27 \text{ V}$$

Now shorting the  $V_{CE(\text{sat})}$  source, the resultant circuit is as shown in Fig. 8.8(e).

$$V_{B1}(V_{CE(\text{sat})} = 0) = -10 \times \frac{10}{110} = \frac{-10}{11} = -0.91 \text{ V}$$

Therefore, the net voltage  $V_{B1}$  at  $B_1$  due to the two sources  $V_{CE(\text{sat})}$  and  $-V_{BB}$  is

$$V_{B1} = 0.27 - 0.91 = -0.64 \text{ V.}$$

This explains that the base of  $Q_1$  is negative with respect to the emitter by 0.64 V. Hence, the base-emitter diode is reverse-biased. Therefore,  $Q_1$  is OFF, as assumed. Hence,  $V_{C1} = V_{CC} = 10 \text{ V}$ . The voltage across the capacitor terminals is

$$V_A = V_{C1} - V_{B2} = V_{CC} - V_{\sigma} = 10 \text{ V} - 0.7 \text{ V} = 9.3 \text{ V}$$

In the stable state, the voltages are  $V_{B1} = -0.64 \text{ V}$ ,  $V_{C1} = 10 \text{ V}$ ,  $V_{B2} = 0.7 \text{ V}$ ,  $V_{C2} = 0.3 \text{ V}$ ,  $V_A = 9.3 \text{ V}$ .

ii) In the quasi-stable state ( $t = 0+$ )

In the quasi-stable state,  $Q_2$  is driven into the OFF state, by the application of a trigger. Consequently,  $Q_1$  goes into the ON state and into saturation as shown in Fig. 8.8(f).

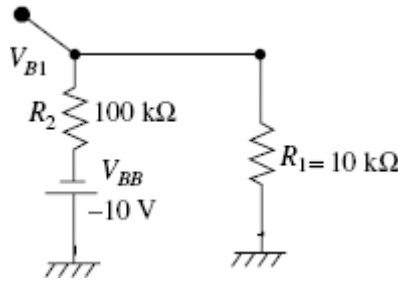


FIGURE 8.8(e) Circuit to calculate  $V_{B1}$  due to  $-V_{BB}$  source

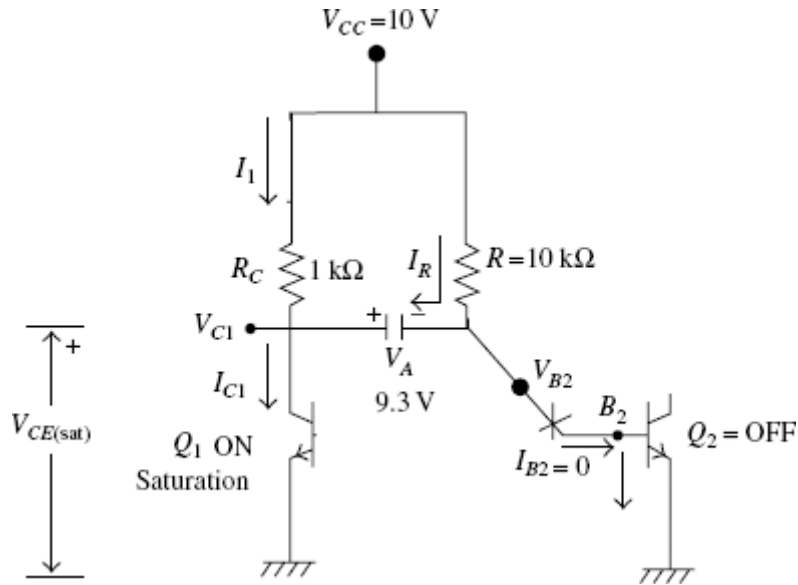


FIGURE 8.8(f) In the quasi-stable state,  $Q_1$  is ON and  $Q_2$  is OFF

a) To verify if  $Q_1$  is ON and in saturation or not

To verify whether  $Q_1$  is really in saturation or not, calculate  $I_{C1}$ .

$$I_{C1} = I_1 + I_R \quad I_1 = \frac{V_{CC} - V_{CE(sat)}}{R_C} = \frac{10 - 0.3}{1 \text{ k}\Omega} = 9.7 \text{ mA}$$

To calculate  $I_R$  the KVL equation of the loop consisting of  $R_C$ ,  $C$  and  $R$  is,

$$I_R R = I_1 R_C + V_A = 9.7 \text{ V} + 9.3 \text{ V} = 19 \text{ V} \quad I_R = \frac{19 \text{ V}}{10 \text{ k}\Omega} = 1.9 \text{ mA}$$

Therefore,

$$I_{C1} = I_1 + I_R = 9.7 \text{ mA} + 1.9 \text{ mA} = 11.6 \text{ mA}$$

$$I_{B1(\min)} = \frac{I_{C1}}{h_{FE \min}} = \frac{11.6 \text{ mA}}{30} = 0.39 \text{ mA}$$

To calculate  $I_{B1}$ , consider Fig. 8.8(g).

$$I_{B1} = I_3 - I_4$$

$$I_3 = \frac{V_{CC} - V_{\sigma}}{R_C + R_1} = \frac{10 - 0.7}{1 + 10} = \frac{9.3 \text{ V}}{11 \text{ k}\Omega} = 0.84 \text{ mA}$$

$$I_4 = \frac{V_{\sigma} - (-V_{BB})}{R_2} = \frac{0.7 + 10}{100 \text{ k}\Omega} = \frac{10.7 \text{ V}}{100 \text{ k}\Omega} = 0.11 \text{ mA}$$

$$I_{B1} = 0.84 - 0.11 = 0.73 \text{ mA}$$

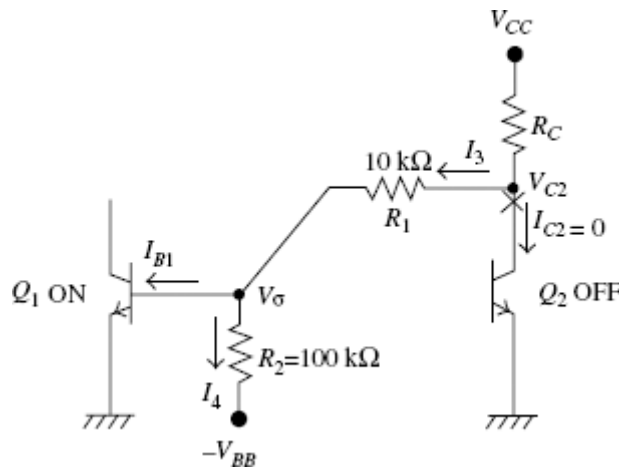


FIGURE 8.8(g) The circuit that is used to calculate  $I_{B1}$

As already calculated,  $I_{B1(\min)} = 0.39 \text{ mA}$ . Thus,  $I_{B1} \gg I_{B1(\min)}$ .

Hence,  $Q_1$  is in saturation.

$$\therefore V_{C1} = 0.3 \text{ V}, V_{B1} = 0.7 \text{ V},$$

$$V_{C2} = V_{CC} - I_3 R_C = 10 - (0.84)(1) = 9.16 \text{ V (But for the current, } I_3, V_{C2} \text{ should have been 10 V)}$$


$$V_{B2} = V_{CC} - I_R R = 10 - (1.9)(10) = -9 \text{ V}$$

In the quasi-stable state, except  $V_{B2}$ —which changes exponentially as a function of time—all other voltages remain unaltered. At  $t = T$ , when  $V_{B2} = V_\gamma$ , the quasi-stable state ends and the multivibrator returns to its initial stable condition. The voltages at the beginning of the quasi-stable state are  $V_{C1} = 0.3 \text{ V}$ ,  $V_{B1} = 0.7 \text{ V}$ ,  $V_{C2} = 9.16 \text{ V}$ ,  $V_{B2} = -9 \text{ V}$  initially and varies exponentially.


iii) At the end of the quasi-stable state (at  $t = T +$ )

At the end of the quasi-stable state  $Q_1$  goes OFF and  $Q_2$  goes ON and into saturation, resulting in overshoots at the base of  $Q_2$  and at the collector of  $Q_1$ . The overshoots are calculated using Fig. 8.8(h).


Neglecting the current  $I_R$  when compared to  $I'_{B2}$  the circuit reduces to Fig. 8.8(i).

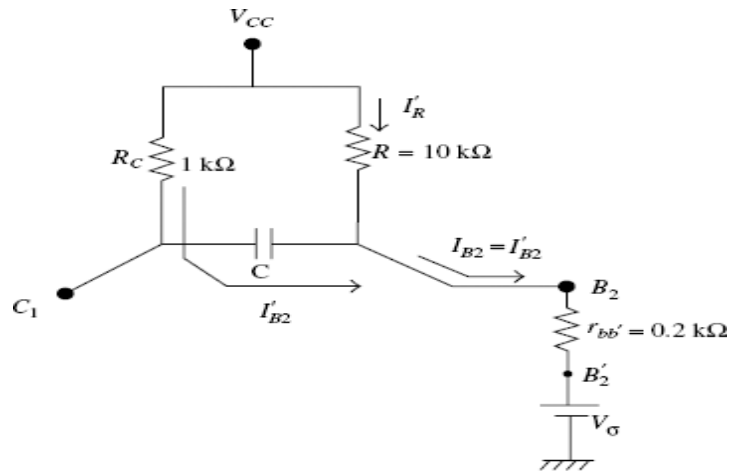

**FIGURE 8.8(h)** The circuit that is used to calculate  $I_{B1}$

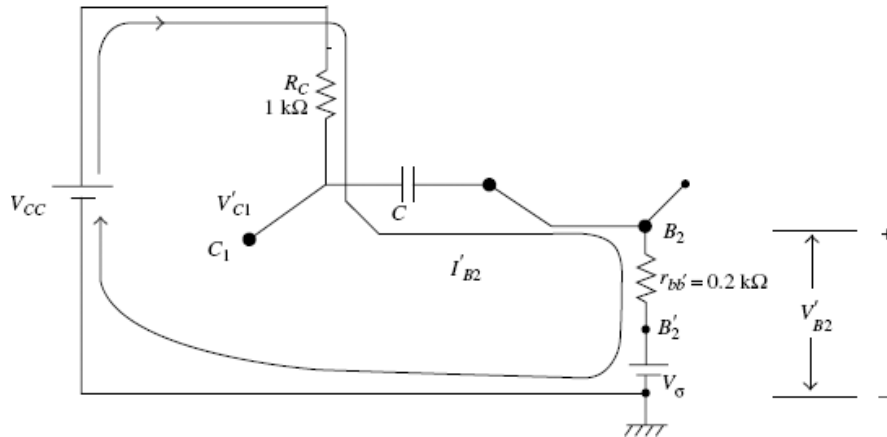

**FIGURE 8.8(i)** The simplified circuit of Fig. 8.8(h)

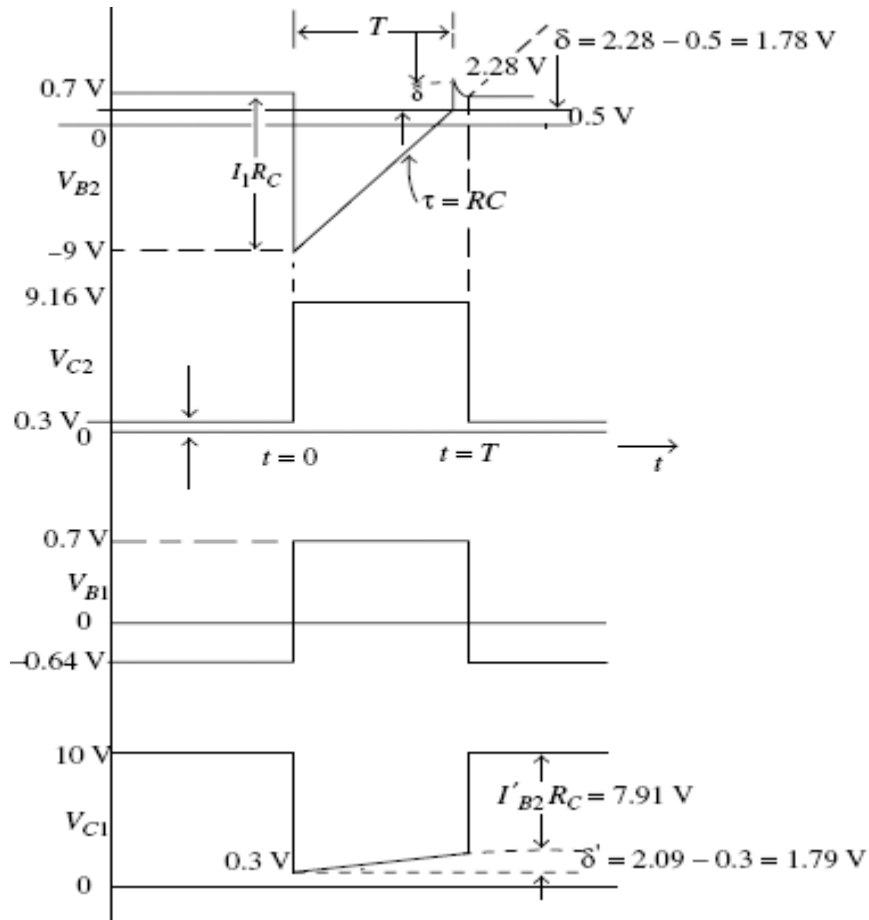

**FIGURE 8.8(j)** Waveforms of the collector-coupled monostable

Using Eq. (8.34):

$$I'_{B2} = \frac{V_{CC} - V_{CE(\text{sat})} - V_{\sigma} + V_{\gamma}}{r_{bb'} + R_C}$$

$$= \frac{10 - 0.3 - 0.7 + 0.5}{0.2 + 1} = \frac{9.5 \text{ V}}{1.2 \text{ k}\Omega}$$

$$I'_{B2} = 7.91 \text{ mA}$$

$$V'_{C1} = V_{CC} - I'_{B2} R_C = 10 - (7.91)(1)$$

$$V'_{C1} = 2.09 \text{ V}$$

$$V'_{B2} = I'_{B2} r_{bb'} + V_{\sigma}$$

$$= (7.91)(0.2) + 0.7 = 1.58 + 0.7$$

$$V'_{B2} = 2.28 \text{ V}$$



At  $t = T^+$ , the voltages are  $V_{C2} = 0.3 \text{ V}$ ,  $V_{B2} = 2.28 \text{ V}$ ,  $V_{C1} = 10 \text{ V}$ ,  $V_{B1} = -0.64 \text{ V}$ . The waveforms are plotted as shown in Fig. 8.8(j).

**Example 8.3:** Design a collector-coupled monostable circuit of Fig. 8.1 to generate a pulse of width  $100 \mu\text{s}$ . Silicon devices with  $h_{FE(\min)} = 50$  are used. ON device is in saturation.

Given that:

$V_{CC} = 12 \text{ V}$ ,  $V_{CE(\text{sat})} = 0.2 \text{ V}$ ,  $V_{BE(\text{sat})} = 0.7 \text{ V}$ ,  $I_{B(\text{sat})} = 2 I_{B(\min)}$ ,  $V_{BB} = 12 \text{ V}$ ,  $I_{C(\text{sat})} = 2 \text{ mA}$ ,  $T = 100 \mu\text{s}$ .

**Solution:**

1. Let  $Q_2$  be ON and  $Q_1$  be OFF.

$$R_{C2} = \frac{V_{CC} - V_{CE(\text{sat})}}{I_{C2(\text{sat})}} = \frac{12 - 0.2}{2 \text{ mA}} = \frac{11.8}{2 \text{ mA}} = 5.9 \text{ k}\Omega \approx 6 \text{ k}\Omega$$

$$I_{B2(\min)} = \frac{I_{C2(\text{sat})}}{h_{FE(\min)}} = \frac{2 \text{ mA}}{50} = 40 \mu\text{A}$$

$$I_{B2(\text{sat})} = 2 \times I_{B2(\min)} = 2 \times 40 = 80 \mu\text{A}$$

$$R = \frac{V_{CC} - V_{\sigma}}{I_{B2(\text{sat})}} = \frac{12 - 0.7}{80 \mu\text{A}} = \frac{11.3}{80 \times 10^{-6}} = \frac{1130}{8} \times 10^3 = 141 \text{ k}\Omega$$

$$h_{FE} R_C = 50 \times 6 = 300 \text{ k}\Omega$$

For ON device to be in saturation,

$$R \leq h_{FE} R_C$$

Hence, the condition is verified.

2. When  $Q_1$  is ON, let  $I_2$  be the current in  $R_2$ .

$$I_2 \approx \frac{1}{10} I_{C(\text{sat})} = 0.2 \text{ mA} \quad R_2 = \frac{V_{\sigma} + V_{BB}}{I_2} = \frac{12.7}{0.2} = 63.5 \text{ k}\Omega$$

Let  $I_1$  be the current in  $R_C + R_1$ .

$$I_1 = I_{B1} + I_2 = 0.08 + 0.2 = 0.28 \text{ mA}$$

$$R_C + R_1 = \frac{V_{CC} - V_{\sigma}}{I_1} = \frac{12 - 0.7}{0.28 \text{ mA}} = 40 \text{ k}\Omega$$

$$R_1 = (R_C + R_1) - R_C = 40 - 6 = 34 \text{ k}\Omega$$

$$T = 0.69 RC \rightarrow 100 \times 10^{-6} \text{ s} = 0.69 \times 141 \times 10^3 \times C$$

$$C = \frac{100 \times 10^{-6}}{0.69 \times 141 \times 10^3} = \frac{100}{7 \times 14} \times 10^{-9} \approx 1 \text{ nF}$$

**Example 8.5:** Design the monostable multivibrator shown in Fig. 8.11(a) having  $V_{CC} = 18\text{ V}$  and  $V = 6\text{ V}$ ,  $h_{FE} = 50$ ,  $I_{C(\text{sat})} = 5\text{ mA}$ .

**Solution:**

For  $V$  to be  $6\text{ V}$ , choose  $R_1 = 200\text{ k}\Omega$ ,  $R_2 = 100\text{ k}\Omega$ , (to avoid loading the dc source) and  $C_b = 10\text{ }\mu\text{F}$  (bypass condenser). Given that  $I_{C(\text{sat})} = 5\text{ mA}$ , assume  $Q_1$  is OFF and  $Q_2$  is ON and in saturation, in the stable state.

Let

$$V_{EN} = V_{EN2} = \frac{V_{CC}}{2} = 9\text{ V}$$

Therefore,

$$V_{BE1} = V - V_{EN2} = 6 - 9 = -3\text{ V}$$

Hence,  $Q_1$  is OFF.

$$R_E = \frac{V_{EN2}}{I_E} = \frac{9\text{ V}}{5\text{ mA}} = 1.8\text{ k}\Omega$$

Choose  $R_E = 2\text{ k}\Omega$

$$R_{C1} = R_{C2} = \frac{V_{CC} - V_{CE(\text{sat})} - V_{EN2}}{I_{C2}} = \frac{18 - 0.2 - 9}{5\text{ mA}} = \frac{8.8\text{ V}}{5\text{ mA}} = 1.75\text{ k}\Omega$$

$$I_{B2(\text{min})} = \frac{I_{C2}}{h_{FE(\text{min})}} = 0.1\text{ mA}$$

Let

$$I_{B2} = 1.5 \times I_{B2(\text{min})} = 0.15\text{ mA}$$

$$R = \frac{V_{CC} - V_{\sigma} - V_{EN2}}{I_{B2}} = \frac{18 - 0.7 - 9}{0.15\text{ mA}} = \frac{8.3\text{ V}}{0.15\text{ mA}} \approx 55\text{ k}\Omega$$

Choose  $R \approx 60\text{ k}\Omega$

**Example 8.6:** For the monostable multivibrator shown in Fig. 8.1,  $R_1 = R_2 = R = 20\text{ k}\Omega$ ,  $C = 0.01\text{ }\mu\text{F}$ ,  $R_C = 2\text{ k}\Omega$ ,  $V_{CC} = 12\text{ V}$ ,  $V_{BB} = -12\text{ V}$ . Find the time period  $T$ .

**Solution:**

$$\text{Time period } T = 0.69RC = 0.69 \times 20 \times 10^3 \times 0.01 \times 10^{-6} = 138\text{ }\mu\text{s}$$

**Example 8.9:** Design a collector-coupled monostable multivibrator shown in Fig. 8.15(a) to obtain an output pulse of amplitude 10 V. Given that  $I_{C(sat)} = 10 \text{ mA}$ ,  $I_{B2} = 2I_{B2(min)}$ ,  $V_{CE(sat)} = 0.1 \text{ V}$ ,  $V_{BE(sat)} = 0.3 \text{ V}$ ,  $h_{FE(min)} = 40$  and a pulse of duration  $1000 \mu\text{s}$  is required.  $V_{BE(\text{cut-off})} = -1 \text{ V}$

**Solution:**


As the pulse amplitude is 10 V, choose  $V_{CC} = 10 \text{ V}$ .

$$R_C = \frac{V_{CC} - V_{CE(sat)}}{I_{C(sat)}} = \frac{10 - 0.1}{10 \text{ mA}} = \frac{9.9 \text{ V}}{10 \text{ mA}} = 990 \Omega$$

Choosing  $R_C = 1 \text{ k}\Omega$ :

$$R = \frac{V_{CC} - V_{\sigma}}{I_{B2}}$$

$$I_{B2(min)} = \frac{I_{C(sat)}}{h_{FE(min)}} = \frac{10 \text{ mA}}{40} = 0.25 \text{ mA}$$

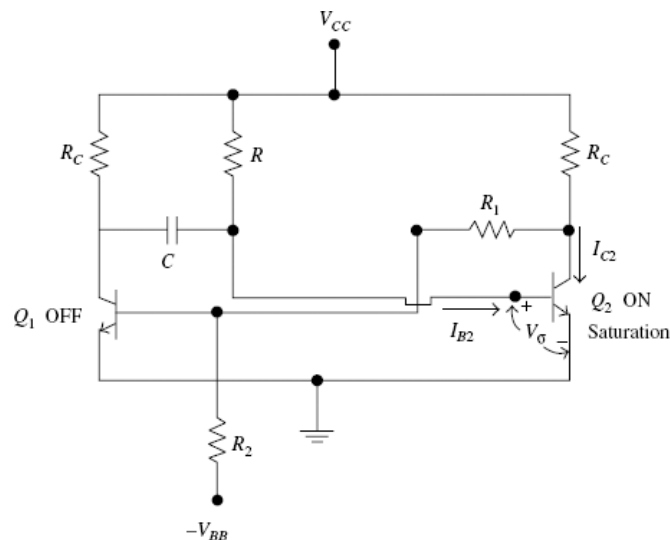

**FIGURE 8.15(a)** The given circuit of the monostable multivibrator

We want,

$$I_{B2} = 2 \times I_{B2(min)} = 2 \times 0.25 = 0.5 \text{ mA}$$

Therefore,

$$R = \frac{10 - 0.3}{0.5} = \frac{9.7 \text{ V}}{0.5 \text{ mA}} = 19.4 \text{ k}\Omega.$$

Choose  $R = 20 \text{ k}\Omega$

$$T = 0.69RC$$

$$1000 \times 10^{-6} = 0.69 \times 20 \times 10^3 \times C$$

Therefore,

$$C = \frac{10^{-6}}{13.8} = 0.072 \mu\text{F}$$

For the value of  $V_{BB}$  to be fixed, consider the Fig. 8.15(b).

If  $V_{BE(\text{cut-off})} = -1 \text{ V}$

$$I_2 = \frac{V_{CE(\text{sat})} - (-V_{BB})}{R_1 + R_2}$$

If  $R_1 = R_2 = R$

$$I_2 = \frac{0.1 + V_{BB}}{2R}$$

Also:

$$I_2 = \frac{V_{B1} - (-V_{BB})}{R_2} \quad I_2 = \frac{-1 + V_{BB}}{R_2}$$

$$\therefore \frac{0.1 + V_{BB}}{2R} = \frac{-1 + V_{BB}}{R}$$

$$0.1 + V_{BB} = 2(-1 + V_{BB})$$

$$0.1 + V_{BB} = -2 + 2V_{BB} \quad V_{BB} = 2.1 \text{ V}$$

To find  $R_1 = R_2$ ,

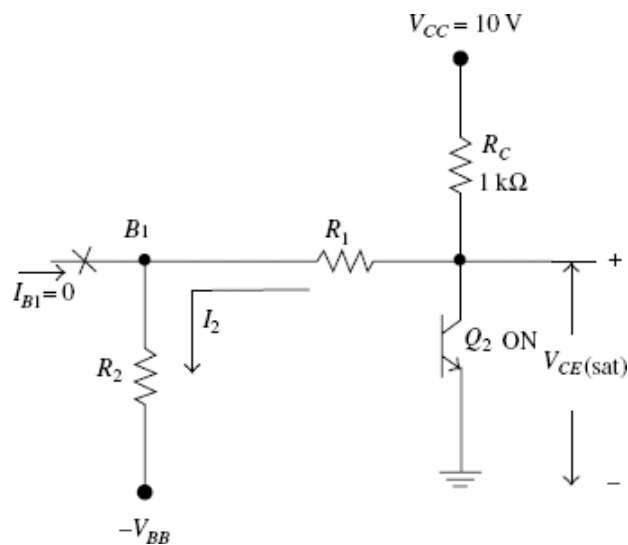


FIGURE 8.15(b) The circuit to calculate  $V_{BB}$

$$I_2 = \frac{1}{10} I_{C(\text{sat})} = \frac{10}{10} = 1 \text{ mA}$$

Therefore,

$$R_1 + R_2 = \frac{V_{CE(\text{sat})} + V_{BB}}{I_2} = \frac{0.1 + 2.1}{1 \text{ mA}} = 2.2 \text{ k}\Omega$$

$$R_1 = R_2 = 1.1 \text{ k}\Omega.$$

**Example 8.10:** Design the circuit for the collector-coupled monostable multivibrator shown in Fig. 8.16. Given that:  $I_{C(\text{sat})} = 5 \text{ mA}$ ,  $V_{B(\text{OFF})} = -1.5 \text{ V}$ ,  $C_i = 20 \text{ pF}$ . It is required to generate a pulse having a width of  $5000 \mu\text{s}$ .  $I_{B(\text{sat})} = 1.5 \times I_{B(\text{min})}$ . Neglect junction voltages and assume  $h_{FE}(\text{min}) = 20$ .

**Solution:** We have

$$R_C = \frac{V_{CC} - V_{CE(\text{sat})}}{I_{C(\text{sat})}} = \frac{V_{CC}}{I_{C(\text{sat})}} = \frac{15}{5} = 3 \text{ k}\Omega$$

$$I_{B2(\text{min})} = \frac{I_{C2(\text{sat})}}{h_{FE}} = \frac{5}{20} = 0.25 \text{ mA}.$$

$$I_{B2(\text{sat})} = 1.5 \times I_{B2(\text{min})} = 1.5 \times 0.25 = 0.375 \text{ mA}$$

$$R = \frac{V_{CC} - V_{\sigma}}{I_{B2(\text{sat})}} = \frac{V_{CC}}{I_{B2(\text{sat})}} = \frac{15}{0.375} = 40 \text{ k}\Omega$$

$$R = 40 \text{ k}\Omega$$

Given

$$T = 5000 \mu\text{s} \quad \text{and} \quad T = 0.69RC$$

$$C = \frac{T}{0.69 \times R} = \frac{5000 \times 10^{-6}}{0.69 \times 40 \times 10^3} = 181.16 \text{ nF}$$

Given that

$$V_{B1(\text{OFF})} = -1.5 \text{ V:}$$

$$V_{B1(\text{OFF})} = \frac{V_{CE(\text{sat})} \times R_2}{R_1 + R_2} + \frac{(V_{BB})R_1}{R_1 + R_2} = \frac{(V_{BB})R_1}{R_1 + R_2} \quad \text{as the first term is small.}$$

$$-1.5 = V_{BB} \times \frac{40}{40 + 40} = 0.5 V_{BB}$$

Therefore,

$$V_{BB} = -3 \text{ V}$$

In the quasi-stable state when  $Q_1$  goes into saturation:

$$I_{B1(\text{sat})} = I_1 - I_2$$

Since junction voltages are negligible:

$$I_{B1(\text{sat})} = \frac{V_{CC} - V_{\sigma}}{R_C + R_1} - \frac{V_{\sigma} + V_{BB}}{R_2} = \frac{V_{CC}}{R_C + R_1} - \frac{V_{BB}}{R_2}$$

Since  $R_1 = R_2$ , the above equation reduces to:

$$0.375 = \frac{15}{3 + R_1} - \frac{3}{R_1}$$

$$\therefore 0.375R_1^2 - 10.875R_1 + 9 = 0$$

$$R_1 = \frac{10.8 \pm \sqrt{(10.8)^2 - (4 \times 0.375 \times 9)}}{2 \times 0.375}$$

From this  $R_1 = 28 \text{ k}\Omega$  or  $0.85 \text{ k}\Omega$ .

Choose  $R_1 = R_2 = 28 \text{ k}\Omega$ .

Further, given that  $C_i = 20 \text{ pF}$ :

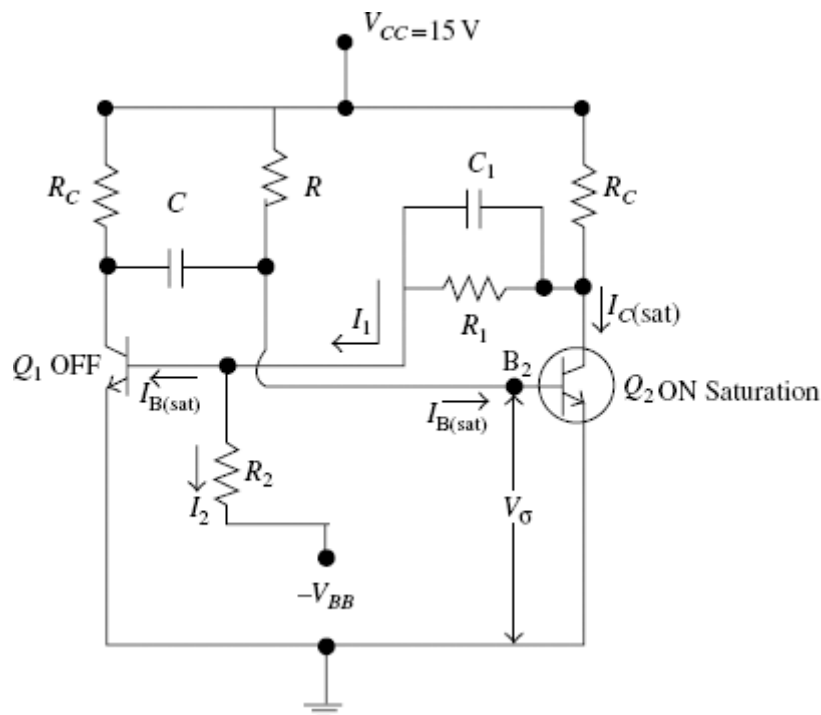


FIGURE 8.16 Monostable multivibrator

Therefore,

$$C_1 = \frac{R_2 C_i}{R_1} = 20 \text{ pF.}$$


In the absence of any specification of  $C_i$ ,  $C_1$  is calculated as  $R_1 C_1 = 1 \mu\text{s}$ .

In which case,

$$C_1 = \frac{1 \times 10^{-6}}{40 \times 10^3} = 25 \text{ pF}$$

## UNSOLVED PROBLEMS

1. A monostable multivibrator is used as a voltage-to-time converter. Find the time period if  $R = 10 \text{ k}\Omega$ ,  $C = 0.01 \mu\text{F}$ ,  $V_{BB}/V_{CC} = 0.5$ .
2. Design a collector-coupled monostable multivibrator using an  $n\text{-p-n}$  silicon transistor with  $h_{FE(\text{min})} = 40$ ,  $V_{BE(\text{cut Off})} \approx 0 \text{ V}$  and  $I_{B(\text{sat})} = 1.5 I_{B(\text{min})}$ . Given that:  $V_{CC} = 10 \text{ V}$ ,  $I_{C(\text{sat})} = 5 \text{ mA}$ ,  $R_{C1} = R_{C2} = R_C$ ,  $V_{CE(\text{sat})} = 0.2 \text{ V}$  and  $V_{BE(\text{sat})} = 0.7 \text{ V}$ . If the pulse width required is  $1 \text{ ms}$ , calculate the value of  $C$ .
3. A collector-coupled monostable multivibrator shown in Fig. 8p.1 using Ge  $n\text{-p-n}$  transistors has the following parameters:  $V_{CC} = 9 \text{ V}$ ,  $V_{BB} = 9 \text{ V}$ ,  $R_C = 2 \text{ k}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$ ,  $R = 10 \text{ k}\Omega$ ,  $h_{FE} = 40$ ,  $r_{bb'} = 0.2 \text{ k}\Omega$ ,  $C = 0.001 \mu\text{F}$ ,  $V_{CE(\text{sat})} = 0.1 \text{ V}$  and  $V_{\sigma} = 0.3 \text{ V}$ .
  - a) Calculate and plot the waveforms.
  - b) Find the pulse width.

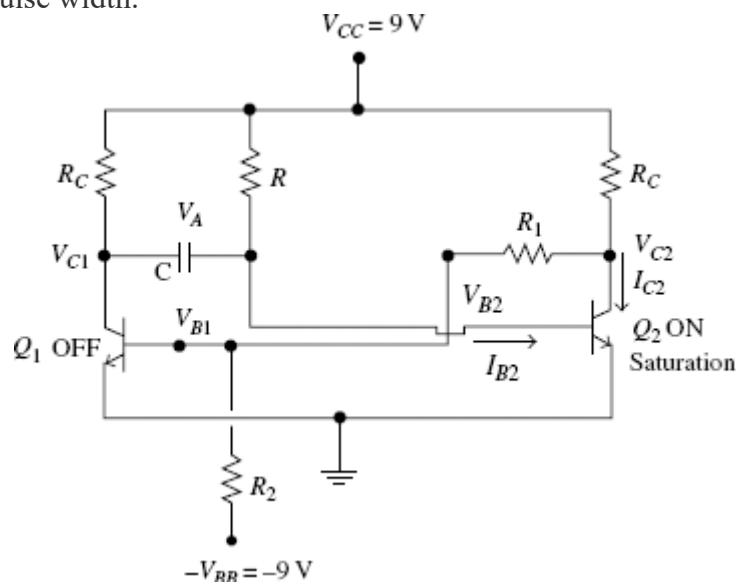

**FIGURE 8p.1** The given circuit of the monostable multivibrator

4. For a collector-coupled monostable multivibrator circuit shown in Fig. 8.1,  $R_1 = R_2 = R = 10 \text{ k}\Omega$ ,  $C = 0.01 \mu\text{F}$ ,  $R_C = 1 \text{ k}\Omega$ ,  $V_{CC} = 10 \text{ V}$ ,  $h_{FE} = 20$ . In the quasi-stable state  $Q_1$  is in the

active region with collector current of 2 mA. Find the time period and the value of  $V_{BB}$ . Neglect junction voltages.  $I_B(\text{sat}) = 1.5 I_{B(\text{min})}$ .

5. An emitter-coupled monostable multivibrator shown in Fig. 8p.2 has the following parameters:  $V_{CC} = 6\text{V}$ ,  $R_{C1} = R_{C2} = R_E = 3\text{ k}\Omega$ ,  $R = 50\text{ k}\Omega$ ,  $V = 2.8\text{ V}$  and  $C = 0.01\text{ }\mu\text{F}$  and  $n\text{-p-n}$  silicon transistors with  $h_{FE} = 50$  and  $r_{bb'} = 100\text{ }\Omega$  are used. A trigger is applied at  $t = 0$ .

- Assume that  $Q_1$  is OFF and  $Q_2$  is ON at  $t = 0^-$ . Calculate the node voltages. Using your calculated values verify that  $Q_1$  is indeed OFF and  $Q_2$  is in saturation.
- Assume that  $Q_1$  is in the active region and  $Q_2$  is OFF at  $t = 0^+$ . Calculate the node voltage and verify that  $Q_1$  is indeed in the active region and  $Q_2$  is OFF.
- Calculate the node voltages at  $t = T^-$ .
- Calculate the node voltages at  $t = T^+$ .

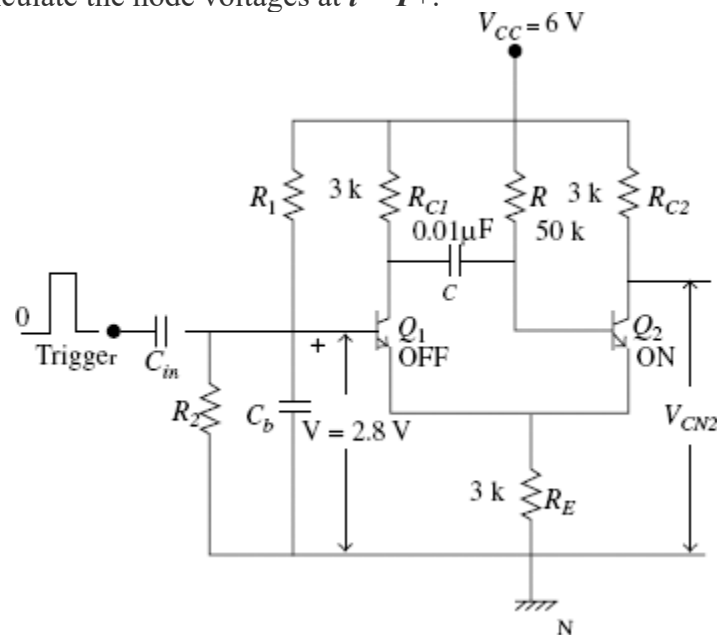


FIGURE 8p.2 Emitter-coupled monostable multivibrator

6. An emitter-coupled monostable multivibrator has the following parameters:  $V_{CC} = 15\text{ V}$ ,  $R_{C1} = R_{C2} = R_E = 4\text{ k}\Omega$ ,  $R = 100\text{ k}\Omega$ ,  $V = 5\text{ V}$  and  $C = 0.01\text{ }\mu\text{F}$  and an  $n\text{-p-n}$  silicon transistor with  $h_{FE(\text{min})} = 40$  and  $r_{bb'} = 100\text{ }\Omega$  is used. Calculate and plot the waveforms to scale.