

A.C. Voltmeter:-

- ① A basic D'Arsonval movement with a full scale deflection of $50\mu A$ & internal resistance of 500Ω is used as a voltmeter. Determine the value of the multiplier resistance needed to measure a voltage range of $0-10V$.

Sol: Given

$$R_s = \frac{V}{I_m} - R_m$$

$$= \frac{10}{50\mu A} - 500$$

$$= 0.2 \times 10^6 - 500$$

$$= 200K - 500$$

$$= 199.5K\Omega$$

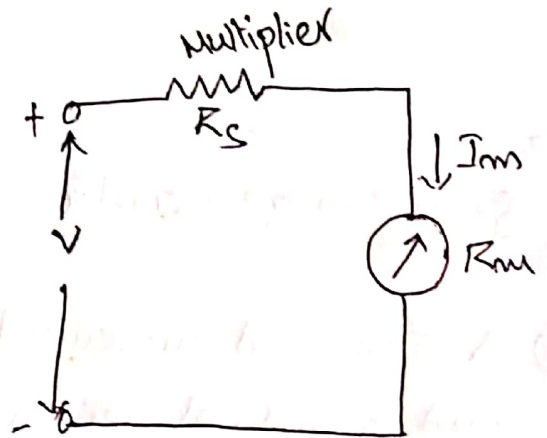


Fig: Basic dc voltmeter

- ② Calculate the value of multiplier resistance on the $50V$ range of a dc voltmeter that uses a $500\mu A$ meter movement with an internal resistance of $1K\Omega$.

Sol: The sensitivity of $500\mu A$ meter movement is given by

$$S = 1/I_m$$

$$= 1/500\mu A$$

$$= 2K\Omega/V$$

The value of the multiplier resistance can be calculated by

$$R_s = S \times \text{range} - R_m$$

$$= 2K\Omega/V \times 50V - 1K\Omega$$

$$= 100K\Omega - 1K\Omega$$

$$= 99K\Omega$$

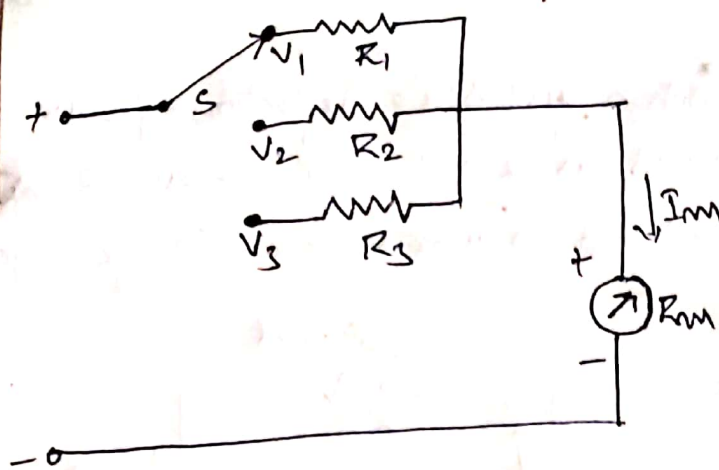


fig: multirange voltmeter

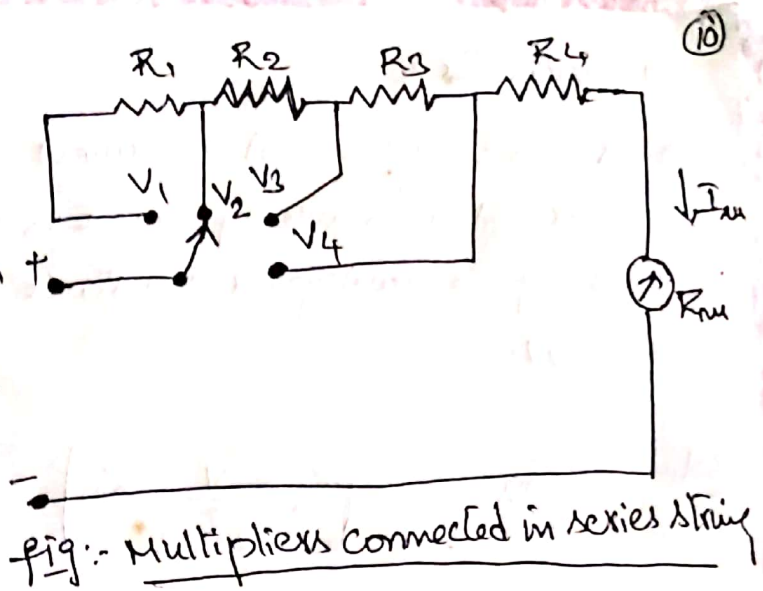


fig: Multipliers connected in series string

③ A D'Arsonval movement with a full scale deflection current of $50\mu A$ & internal resistance of 500Ω is to be converted into a multi-range voltmeter. Determine the value of multiplier required for $0-20V$, $0-50V$ & $0-100V$.

Sol: Given $I_m = 50\mu A$ & $R_m = 500\Omega$

Case 1:- for range $0-20V$

$$R_s = \frac{V}{I_m} - R_m$$

$$= \frac{20}{50 \times 10^{-6}} - 500$$

$$= 0.4 \times 10^6 - 500$$

$$= 400K - 500$$

$$= 399.5K\Omega$$

Case 2:- for range $0-50V$

$$R_s = \frac{V}{I_m} - R_m$$

$$= \frac{50}{50 \times 10^{-6}} - 500$$

$$= 1 \times 10^6 - 500$$

$$= 1000K - 500$$

$$= 999.5K\Omega$$

Case 3:- For range $0-100V$

$$R_s = \frac{V}{I_m} - R_m$$

$$= \frac{100}{50 \times 10^{-6}} - 500$$

$$= 2000K - 500 = 1999.5K\Omega$$

~~Exercise~~ **10mA**
Exercise prob

④ Convert a basic D'Arsonval movement with an internal resistance of 100Ω & a full scale deflection of $10\mu A$ into a multirange dc voltmeter with ranges from $0-5V$, $0-50V$ & $0-100V$. ⑪

Sol: ~~Ref diag~~. Above 2nd diagram is Ref diagram.

Given $I_m = 10\mu A$, $R_m = 100\Omega$

Step 1:- for a $5V$ (V_3) the total ext resistance

$$R_t = \frac{V}{I_{fsd}} = \frac{5}{10\mu A} = 0.5K\Omega$$

$$\therefore R_3 = R_t - R_m$$

$$= 500\Omega - 100\Omega$$

$$= 400\Omega$$

Step 2:- for a $50V$ (V_2) position

$$R_t = \frac{V}{I_{fsd}}$$

$$= \frac{50}{10\mu A}$$

$$= 5K\Omega$$

$$\therefore R_2 = R_t - (R_3 + R_m)$$

$$= 5K\Omega - (400\Omega + 100\Omega)$$

$$= 5K\Omega - 500\Omega$$

$$= 4.5K\Omega$$

Step 3:- for a $100V$ range (V_1) position

$$R_t = \frac{V}{I_{fsd}} = \frac{100}{10\mu A} = 10K\Omega ; \therefore R_1 = R_t - (R_2 + R_3 + R_m)$$

$$= 10K\Omega - (4.5K\Omega + 400\Omega + 100\Omega)$$

$$= 5K\Omega$$


⑤ Calculate the value of multiplier resistance for the multiple range dc voltmeter Ckt is shown. (12)

Sol: The sensitivity of the meter movement is given as follows.

$$S = \frac{1}{I_{fsd}}$$

$$= \frac{1}{50\mu A}$$

$$= 20K\Omega/V$$

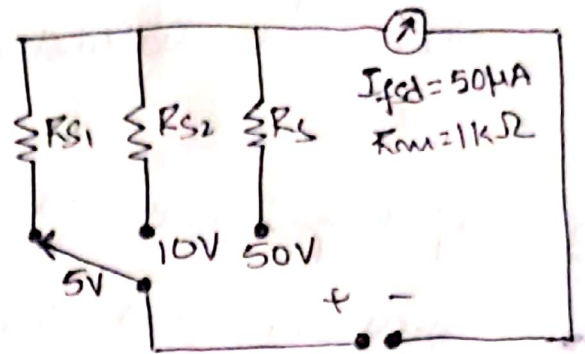

The value of the multiplier resistance can be calculated as follows for 5V range

$$R_{s1} = S \times V - R_m$$

$$= 20K \times 5 - 1K$$

$$= 100K - 1K$$

$$= \underline{99K\Omega}$$

Example probe

$$R_{s1} = 3V$$

$$R_{s2} = 10V$$

$$R_{s3} = 30V$$

for 10V range $R_{s2} = S \times V - R_m$

$$= 20K \times 10 - 1K$$

$$= 200K - 1K$$

$$= \underline{199K\Omega}$$

for 50V range

$$R_{s3} = S \times V - R_m$$

$$= 20K \times 50 - 1K$$

$$= 1000K - 1K$$

$$= \underline{999K\Omega}$$

$$\underline{R_{s1}}: 59K\Omega$$

$$199K\Omega$$

$$999K\Omega$$