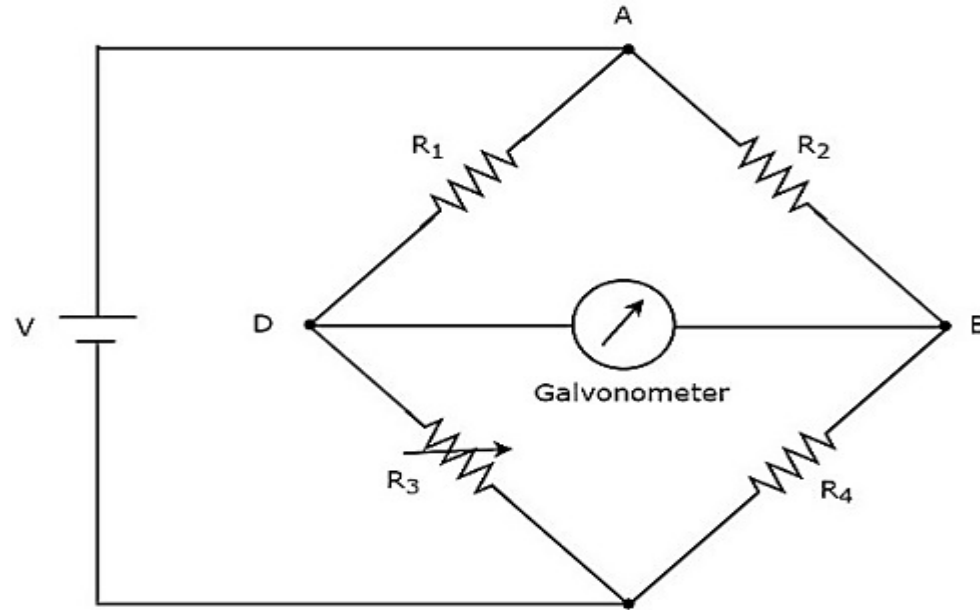


UNIT-4

BRIDGES

Types of Bridges:-

- If the electrical components are arranged in the form a bridge or ring structure, then that electrical circuit is called a **bridge**. In general, bridge forms a loop with a set of four arms or branches. Each branch may contain one or two electrical components.
- We can classify the bridge circuits or bridges into the following two categories based on the voltage signal with which those can be operated.
 - (I) DC Bridges
 - (II) AC Bridges
- **DC Bridges:-**
 - If the bridge circuit can be operated with only DC voltage signal, then it is a DC bridge circuit or simply **DC bridge**. DC bridges are used to measure the value of unknown resistance. The **circuit diagram** of DC bridge looks like as shown in below figure.



The above DC bridge has **four arms** and each arm consists of a resistor. Among which, two resistors have fixed resistance values, one resistor is a variable resistor and the other one has an unknown resistance value.


The above DC bridge circuit can be excited with a **DC voltage source** by placing it in one diagonal. The galvanometer is placed in other diagonal of DC bridge. It shows some deflection as long as the bridge is unbalanced.

Vary the resistance value of variable resistor until the galvanometer shows null (zero) deflection. Now, the above DC bridge is said to be a balanced one. So, we can find the value of **unknown resistance** by using nodal equations.

AC Bridges:-

If the bridge circuit can be operated with only AC voltage signal, then it is said to be AC bridge circuit or simply **AC bridge**.

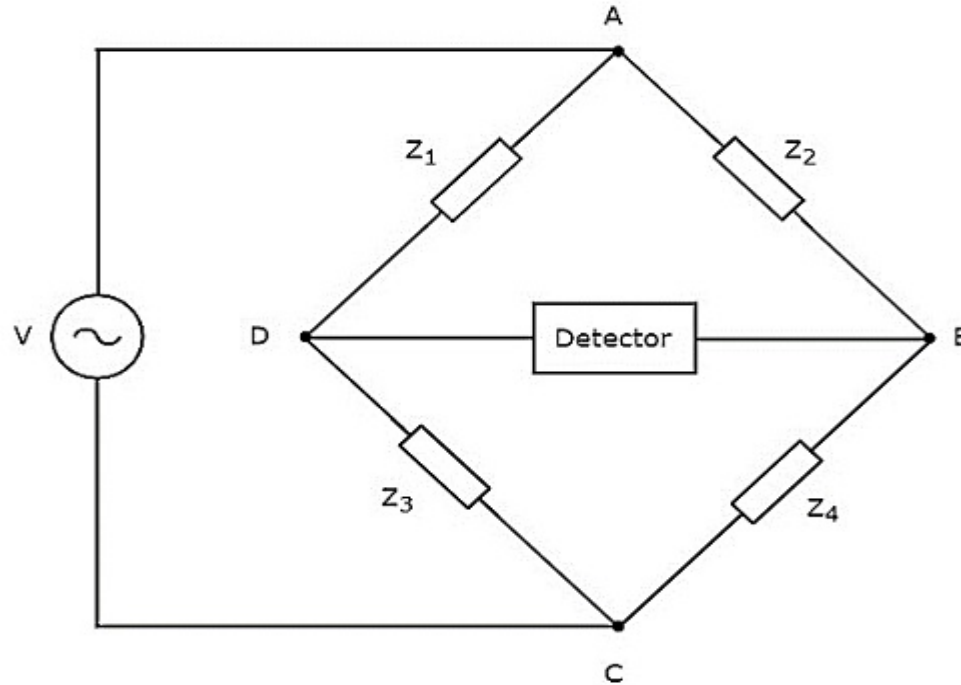AC bridges are used to measure the value of unknown inductance, capacitance and frequency. The **circuit diagram** of AC bridge looks like as shown in below figure.



The circuit diagram of AC bridge is similar to that of DC bridge. The above AC bridge has **four arms** and each arm consists of some impedance. That means, each arm will be having either single or combination of passive elements such as resistor, inductor and capacitor.

Among the four impedances, two impedances have fixed values, one impedance is variable and the other one is an unknown impedance.

The above AC bridge circuit can be excited with an **AC voltage source** by placing it in one diagonal. A detector is placed in other diagonal of AC bridge. It shows some deflection as long as the bridge is unbalanced.

The above AC bridge circuit can be excited with an **AC voltage source** by placing it in one diagonal. A detector is placed in other diagonal of AC bridge. It shows some deflection as long as the bridge is unbalanced.

Vary the impedance value of variable impedance until the detector shows null (zero) deflection. Now, the above AC bridge is said to be a balanced one. So, we can find the value of **unknown impedance** by using balanced condition.

DC bridges can be operated with only DC voltage signal. DC bridges are useful for measuring the value of unknown resistance, which is present in the bridge. Wheatstone's Bridge is an example of DC bridge.

Maxwells Bridge Definition:-

Maxwell's bridge is also known as Maxwell's Wein bridge or modified form of [Wheatstone bridge](#) or Maxwell's inductance capacitance bridge, consists of four arms used to measure unknown inductances in terms of calibrated capacitances and resistances.

It can be used to measure unknown inductance value and compares it with the standard value. It works on the principle of comparison of known and unknown inductance values.

It uses the null deflection method to calculate inductance with a parallel calibrated [resistor](#) and capacitor. The Maxwell's bridge circuit is said to be in resonance if the positive phase angle of an inductive impedance is compensated with the negative phase angle of the capacitive impedance (connected in the opposite arm). Hence there will be no current flowing through the circuit and no potential across the null detector.

Maxwells Bridge Formula

If the maxwell's bridge is in balance condition, the unknown inductance can be measured by using a variable standard capacitor. The maxwell's bridge formula is given as (in terms of inductance, resistance, and capacitance)

$$R_1 = R_2 r_3 / R_4$$


$$L_1 = R_2 R_3 C_4$$

The quality factor of Maxwell's bridge circuit is given as,

$$Q = \omega L_1 / R_1 = \omega C_4 R_4$$

Maxwells Bridge Circuit

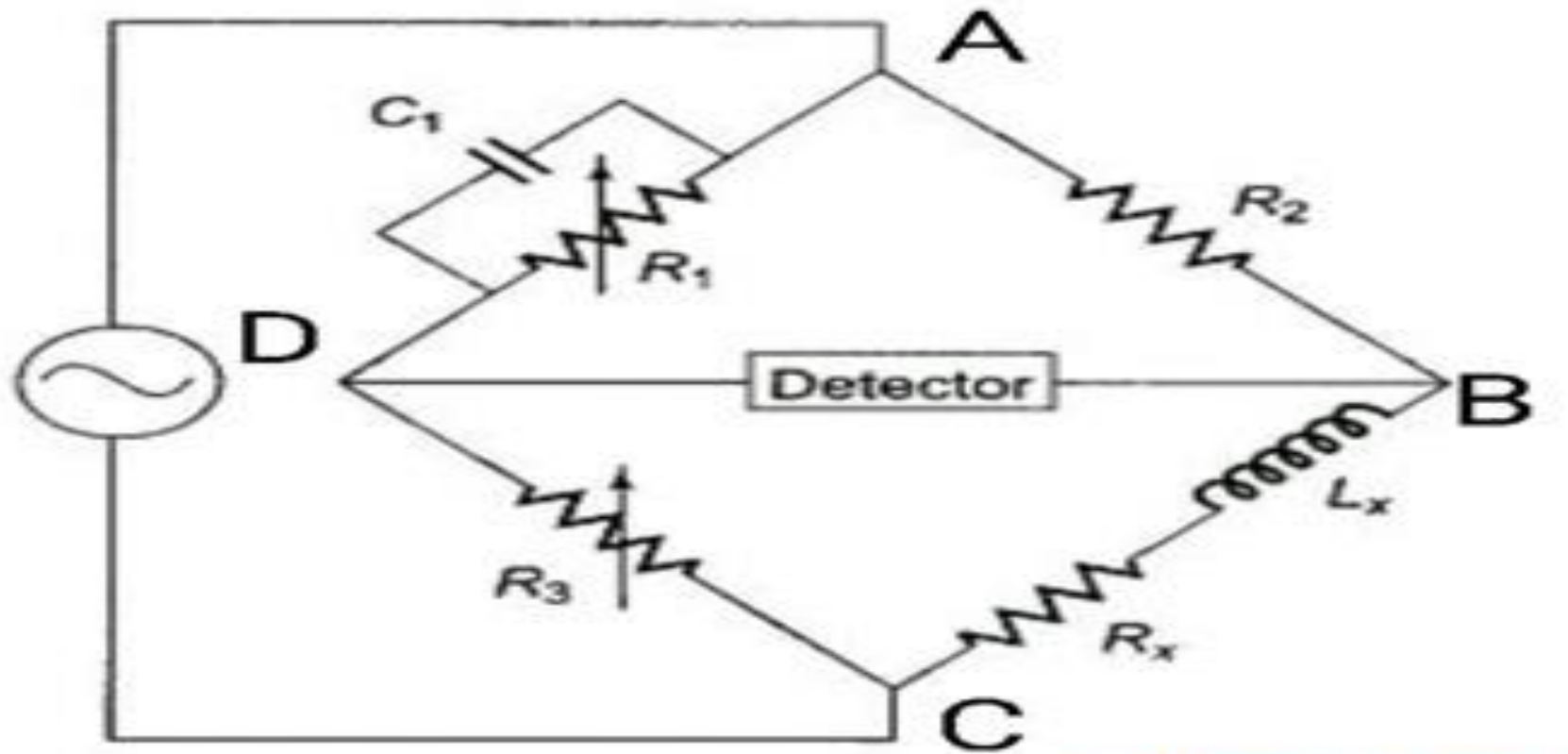Maxwell's bridge circuit consists of 4 arms connected in square or rhombus shape. In this circuit, two arms contain a single resistor, another one arm contains a resistor and inductor in series combination, and the last arm contains a resistor and capacitor in parallel combination. The basic Maxwell's bridge circuit is shown below.



An AC voltage source and a null detector are connected in diagonal to the bridge circuit to measure the unknown inductance value and compared with the known values.

Maxwells Bridge Equation

From the circuit, AB, BC, CD, and DA are the 4 arms connected in rhombus shape.

AB and CD are the resistors R_2 and R_3 ,

BC is a series combination of resistor and inductor given as R_x and L_x .

DA is a parallel combination of resistor and capacitor given as R_1 and C_1

Consider Z_1 , Z_2 , Z_3 , and Z_X are the impedances of the 4 arms of the bridge circuit. The values for these impedances are given as,

$$Z_1 = (R_1 + j\omega L_1) \text{ [since } Z_1 = R_1 + 1/j\omega C_1 \text{]}$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_X = (R_4 + j\omega L_X)$$

Or

Z1= R1 in parallel with C1 that is, $Y1=1/Z1$

$$\mathbf{Y1 = 1/R1 + j \omega C1}$$

$$\mathbf{Z2=R2}$$

$$\mathbf{Z3=R3}$$

Zx=Rx in series with Lx =Rx+jωLx

Take the balance equation of a basic AC bridge circuit as follows,

$$\mathbf{Z1Zx=Z2Z3}$$

$$\mathbf{Zx=Z2Z3/Z1.....(1)}$$

Substitute the values of impedances of Maxwell's bridge circuit in the above balance equation. Then,

$$\mathbf{Rx+j\omega Lx = R2R3 ((1/R1)+j\omega C1)}$$

$$\mathbf{Rx+j\omega Lx = R2R3/R1+ j\omega C1R2R3}$$

Now equate the real and imaginary terms from the above two equations,

$$R_x = R_2 R_3 / R_1 \text{ and } j\omega L_x = j\omega C_1 R_2 R_3$$

$$R_x = R_2 R_3 / R_1 \text{ and } L_x = C_1 R_2 R_3$$

$$Q = \omega L_x / R_x = \omega C_1 R_2 R_3 \times R_1 / R_2 R_3 = \omega C_1 R_1$$

Where Q = quality factor of the bridge circuit

R_x = unknown resistance

L_x = unknown inductance

R_2 and R_3 = known non-inductive resistances

C_1 = capacitor connected in parallel to the variable resistor R_1

Advantages of Maxwells Bridges:-

- At the balance condition, the bridge circuit is independent of frequency
- It helps to measure a wide range of inductance values at audio and power frequency
- To measure the inductance value directly, the scale of calibrated resistance is used.
- It is used to measure the high range of inductances and compared with a standard value.

Disadvantages of Maxwells Bridge:-

- The fixed capacitor in Maxwell's bridge circuit may create interaction between resistance and reactance balance.
- It is not suitable to measure a high range of quality factor (Q values ≥ 10)
- The variable standard capacitor used in the circuit is very costly.
- It is not used to measure the low-quality factor (Q value) due to the circuit balance condition. Hence it is used for medium quality coils.

Applications of Maxwells Bridge:-

- Used in communication systems
- Used in electronic circuits
- Used in power and audio frequency circuits
- Used to measure unknown inductance values of the circuit and compared with a standard value.
- Used to measure medium quality coils.
- Used in filter circuits, instrumentation, linear and non-linear circuits
- Used in power conversion circuits.

two AC bridges.

- Schering Bridge
- Wien's Bridge


These two bridges can be used to measure capacitance and frequency respectively.

Schering Bridge:-

Schering bridge is an AC bridge having four arms, which are connected in the form of a rhombus or **square shape**, whose one arm consists of a single resistor, one arm consists of a series combination of resistor and capacitor, one arm consists of a single capacitor & the other arm consists of a parallel combination of resistor and capacitor.

The AC detector and AC voltage source are also used to find the value of unknown impedance, hence one of them is placed in one diagonal of Schering bridge and the other one is placed in other diagonal of Schering bridge.

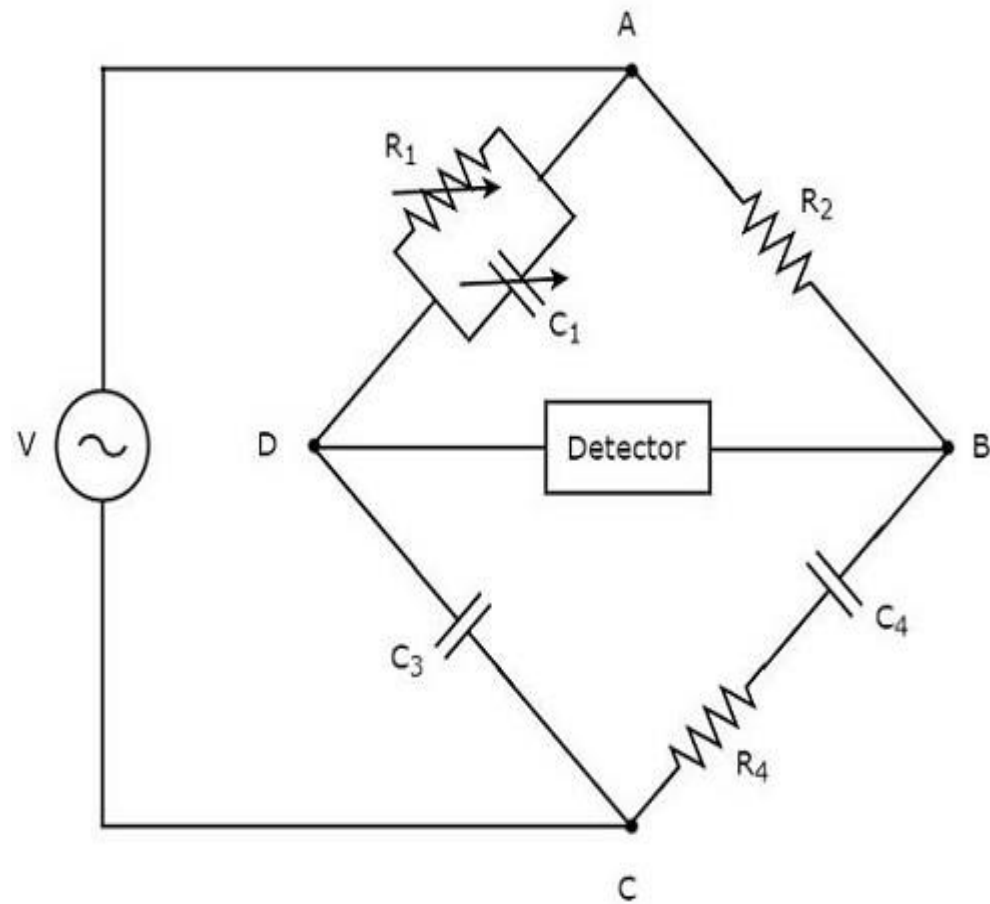Schering bridge is used to measure the value of capacitance. The **circuit diagram** of Schering bridge is shown in the below figure.



the arms AB, BC, CD and DA together form a rhombus or **square shape**.

The arm AB consists of a resistor, R_2 . The arm BC consists of a series combination of resistor, R_4 and capacitor, C_4 .

The arm CD consists of a capacitor, C_3 .

The arm DA consists of a parallel combination of resistor, R_1 and capacitor, C_1 .

Let, Z_1 , Z_2 , Z_3 and Z_4 are the impedances of arms DA, AB, CD and BC respectively. The **values of these impedances** will be

$$Z_1 Z_x = Z_2 Z_3$$

$$Z_x = Z_2 Z_3 / Z_1, \quad Z_x = Z_2 Z_3 Y_1$$

$$Z_x = R_x + 1/j\omega C_x$$

$$Z_x = R_x - j/\omega C_x$$

$$Z_2 = R_2$$

$$Z_3 = 1/j\omega C_3 = -j/\omega C_3$$

$$Y_1 = 1/R_1 + j\omega C_1$$

$$(R_x - j/\omega C_x) = R_2(-j/\omega C_3)(1/R_1 + j\omega C_1)$$

$$= -R_2 j/\omega C_3 R_1 + R_2 \omega C_1 / \omega C_3$$

$$R_x - j/\omega C_x = R_2(-j)/R_1 \omega C_3 + R_2 C_1 / C_3$$

(OR)

$$R_2 C_1 / C_3 - jR_2 / \omega C_3 R_1$$

Now equate the real and imaginary terms

$$R_x = R_2 C_1 / C_3 \text{ and } C_x = R_1 / R_2 * C_3$$

By **comparing** the respective real and imaginary terms of above equation, we will get

$$C_4 = R_1 C_3 / R_2$$

Equation 1

$$R_4 = C_1 R_2 / C_3$$

Equation 2

By substituting the values of R_1, R_2 and C_3 in Equation 1, we will get the value of capacitor, C_4 . Similarly, by substituting the values of R_2, C_1 and C_3 in Equation 2, we will get the value of resistor, R_4 .

The **advantage** of Schering bridge is that both the values of resistor, R_4 and capacitor, C_4 are independent of the value of frequency.

The dial of capacitor C_1 can be calibrated directly to give the dissipation factor at a particular frequency.

The dissipation factor 'D' of a series RC ckt is defined as the cotangent of phase angle

$$D = R_x / X_x = \omega C_x R_x$$

Also, D is the reciprocal of the quality factor Q, i.e., $D = 1/Q$. D indicates the quality of the capacitor.

This bridge is widely used for testing small capacitors at low voltages with very high precision.

WIEN'S BRIDGE:-

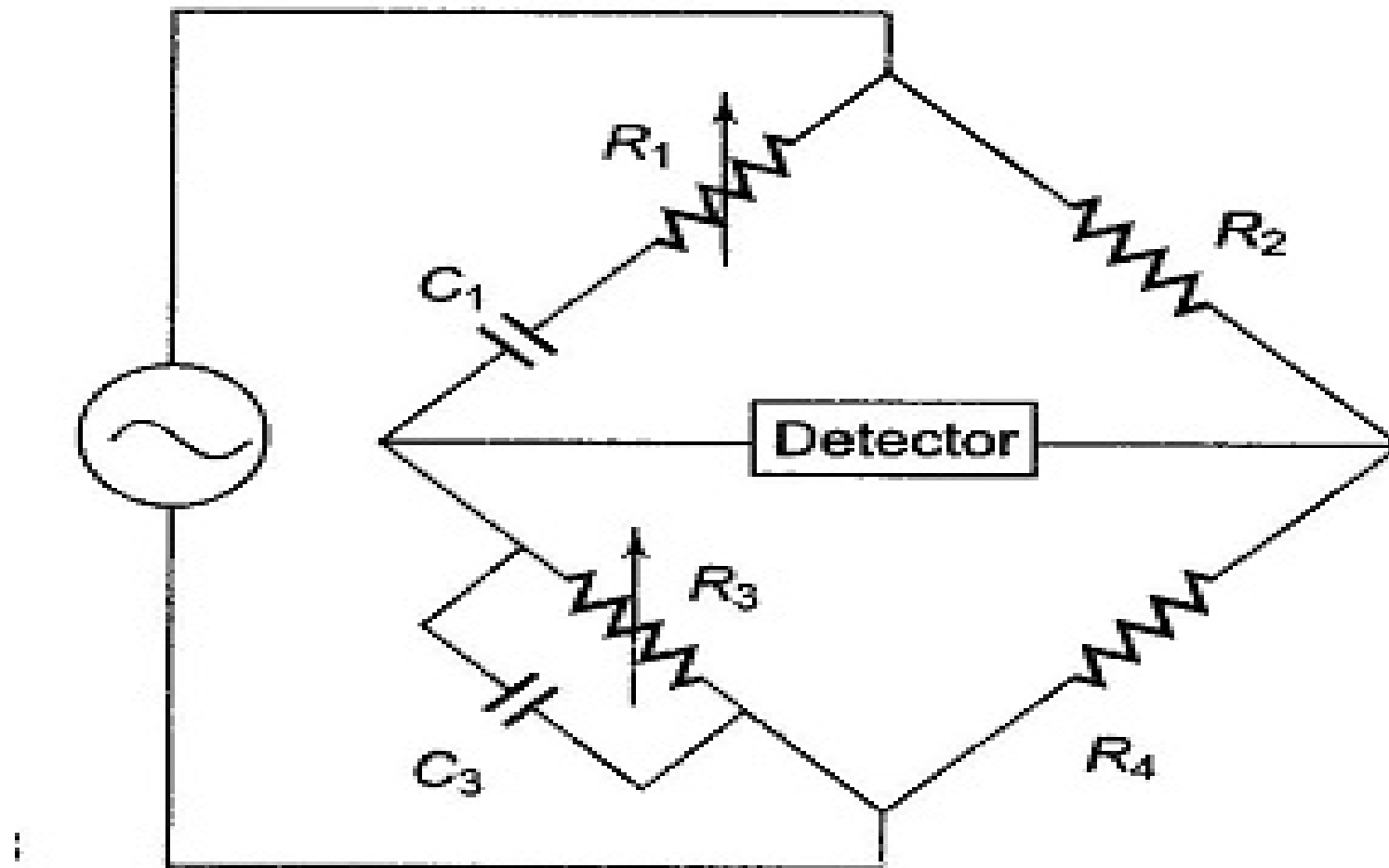


Fig. 11.27

Wien's Bridge

$$Z_1 = R_1 \text{ in series with } C_1 = R_1 - j/\omega C_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3 \text{ in parallel with } C_3 = Y_3 = \frac{1}{R_3} + j\omega C_3$$

$$Z_4 = R_4$$

$$\text{At balanced condition; } \Rightarrow Z_1 Z_4 = Z_2 Z_3$$

$$Z_2 = Z_1 Z_4 / Z_3 \Rightarrow Z_2 = Z_1 Z_4 Y_3$$

$$\begin{aligned} R_2 &= \left(R_1 - \frac{j}{\omega C_1} \right) R_4 \left(\frac{1}{R_3} + j\omega C_3 \right) \\ &= \left(R_1 R_4 - \frac{j R_4}{\omega C_1} \right) \left(\frac{1}{R_3} + j\omega C_3 \right) \\ &= \frac{R_1 R_4}{R_3} - \frac{j R_4}{\omega C_1 R_3} + j\omega C_3 R_1 R_4 - \frac{j^2 \omega C_3 R_4}{\omega C_1} \\ &= \frac{R_1 R_4}{R_3} - \frac{j R_4}{\omega C_1 R_3} + j\omega C_3 R_1 R_4 + \frac{C_3 R_4}{C_1} \end{aligned}$$

Now equate the real and imaginary terms

$$\begin{aligned} R_2 &= \frac{R_1 R_4}{R_3} + \frac{C_3 R_4}{C_1} \\ \frac{R_2}{R_4} &= \frac{R_1}{R_3} + \frac{C_3}{C_1} \quad \& \quad - \frac{j R_4}{\omega C_1 R_3} \\ \frac{R_4}{\omega C_1 R_3} &= \omega C_3 R_1 R_4 \\ \omega^2 &= \frac{1}{C_1 R_1 C_3 R_3} \end{aligned}$$

$$f = \frac{1}{2\pi\sqrt{R_1 C_1 R_3 C_3}}$$

If we assume $C_1 = C_3 = C$; $R_1 = R_3 = R$

$$f = \frac{1}{2\pi\sqrt{R^2 C^2}}$$

$$f = \frac{1}{2\pi RC}$$

Applications of Wien Bridge Oscillators

- It is used to measure the audio frequency.
- Wien bridge oscillator designs the long range of frequencies
- It produces sine wave.

Advantages

- Distortion testing of power amplifier.
- It supplies the signals for testing filters.
- Excitation for AC Bridge.
- To fabricate pure tune.
- Long distance can be spanned by the resting beams.

Disadvantages

- The [Wheatstone bridge](#) is not used for the high resistance.
- The circuit needs the high no. of other components.
- The limited output frequency is obtained because the amplitude and the phase shift characters of the amplifier.

- **ANDERSON BRIDGE:-**

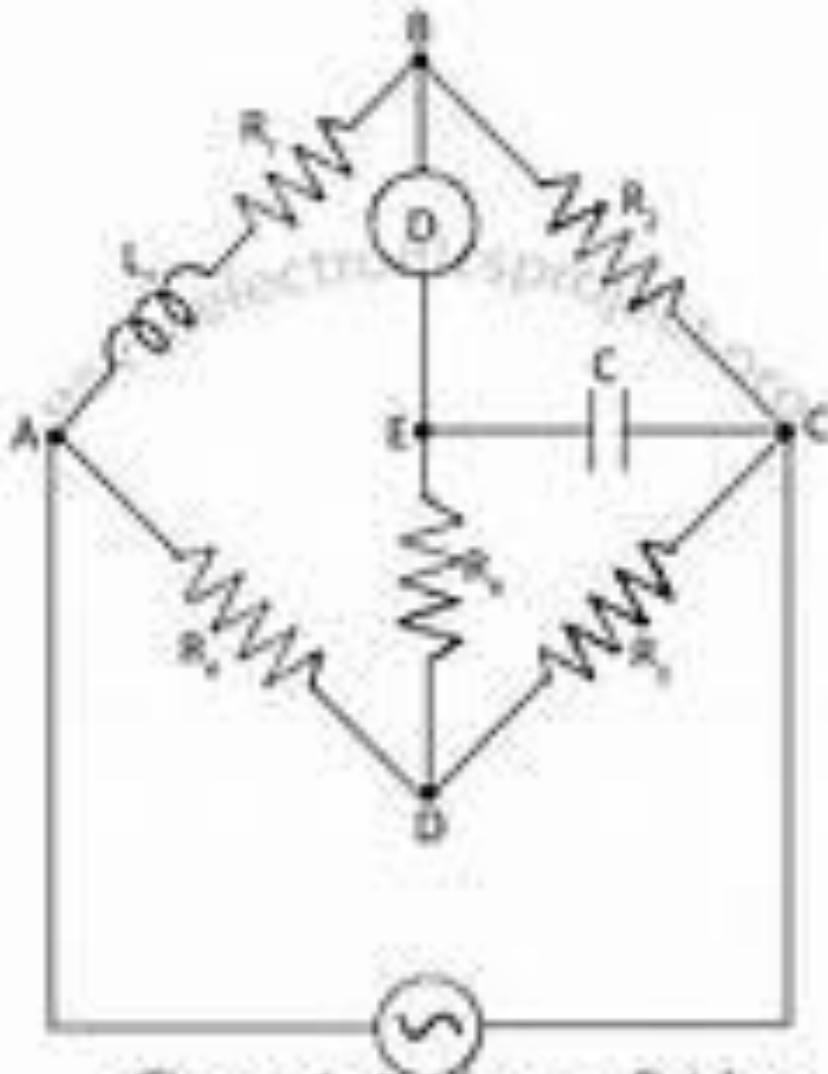


Figure 1: Anderson Bridge


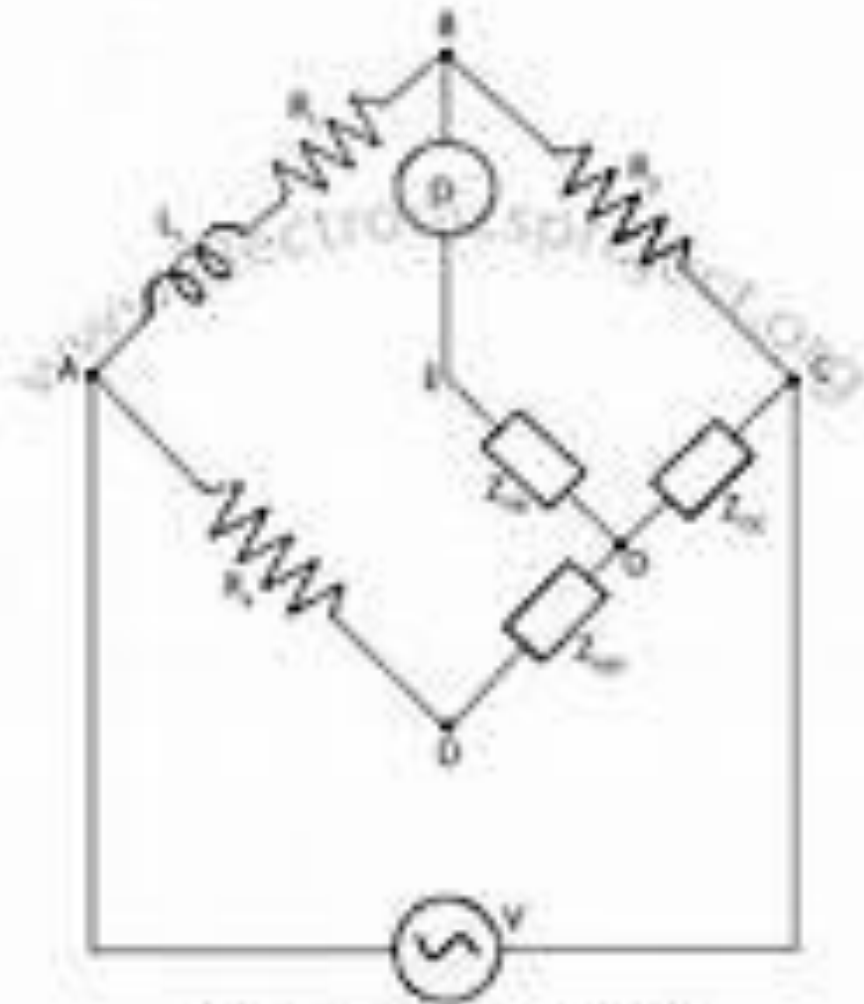


Figure 2: Anderson Bridge


Star to Delta Transformation

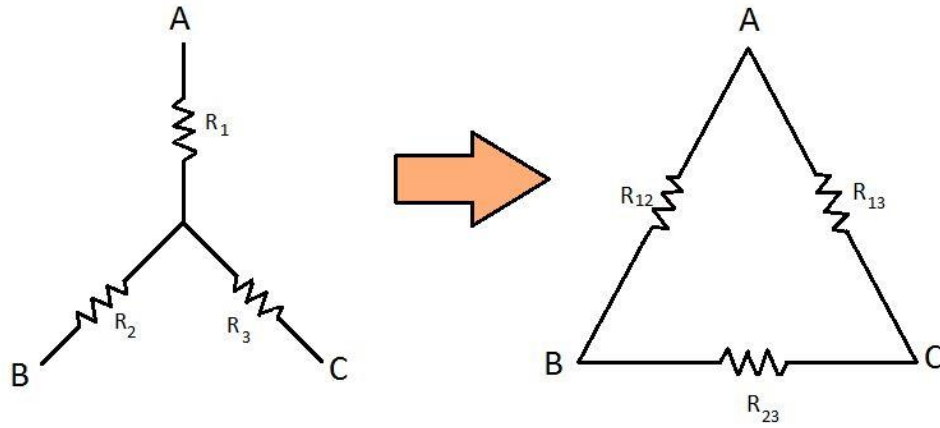

Delta-Star	Star-Delta
$R_1 = \frac{R_{12}R_{13}}{R_{12} + R_{23} + R_{31}}$	$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$
$R_2 = \frac{R_{12}R_{23}}{R_{12} + R_{23} + R_{31}}$	$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$
$R_3 = \frac{R_{23}R_{31}}{R_{12} + R_{23} + R_{31}}$	$R_{31} = R_3 + R_1 + \frac{R_1 R_3}{R_2}$

Star-Delta and Delta-Star Transformations

Delta to Star Transformation

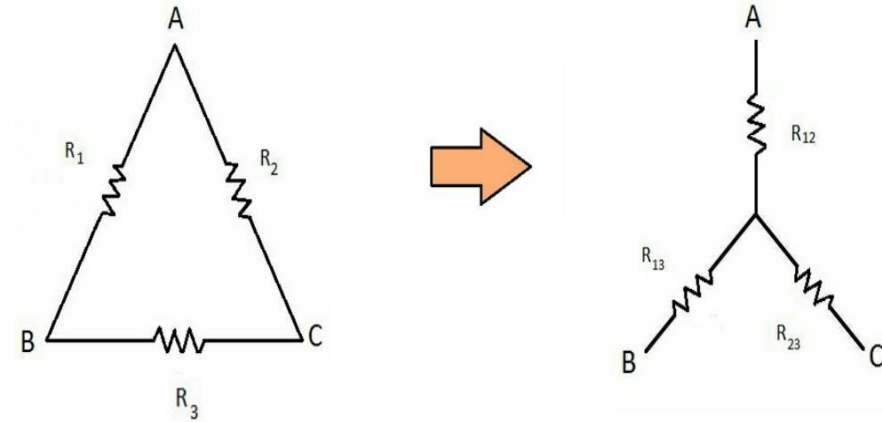

As per delta to star transformation

$$Z_{OD} = \frac{R_3 R_5}{\left(R_3 + R_5 + \frac{1}{j\omega c}\right)} \quad Z_{OC} = \frac{\frac{R_3}{j\omega c}}{\left(R_3 + R_5 + \frac{1}{j\omega c}\right)} = Z_3$$

Hence with reference fig(b) it can be seen that

$$Z_1 = (R_1 + j\omega L_1), Z_2 = R_2, Z_3 = Z_{OC} = \frac{\frac{R_3}{j\omega c}}{\left(R_3 + R_5 + \frac{1}{j\omega c}\right)}, Z_4 = R_2 + Z_{OD}$$

For balance condition

$$Z_1 Z_3 = Z_2 Z_4$$
$$(R_1 + j\omega L_1) \left(\frac{\frac{R_3}{j\omega c}}{R_3 + R_5 + \frac{1}{j\omega c}} \right) = R_2 \left(R_4 + \frac{R_3 R_5}{R_3 + R_5 + \frac{1}{j\omega c}} \right)$$

By simplifying

$$(R_1 + j\omega L_1) \left(\frac{\frac{R_3}{j\omega c}}{R_3 + R_5 + \frac{1}{j\omega c}} \right) = R_2 \left(R_4 \left(R_3 + R_5 + \frac{1}{j\omega c} \right) + \frac{R_3 R_5}{R_3 + R_5 + \frac{1}{j\omega c}} \right)$$

$$(R_1 + j\omega L_1) \times \frac{R_3}{j\omega c} = R_2 R_4 \left(R_3 + R_5 + \frac{1}{j\omega c} \right) + R_2 R_3 R_5$$

$$\frac{R_1 R_3}{j\omega c} + \frac{j\omega L_1 R_3}{j\omega c} = R_2 R_3 R_4 + R_2 R_4 R_5 + \frac{R_1 R_3}{j\omega c} + R_2 R_3 R_5$$

$$-\frac{jR_1 R_3}{\omega c} + \frac{L_1 R_3}{c} = R_2 R_3 R_4 + R_2 R_4 R_5 + R_2 R_3 R_5 - \frac{jR_2 R_4}{\omega c}$$

- Now equate the real and imaginary terms

$$\frac{L_1 R_3}{c} = R_2 R_3 R_4 + R_2 R_4 R_5 + R_2 R_3 R_5$$

$$L_1 = \frac{c}{R_3} (R_2 R_3 R_4 + R_2 R_4 R_5 + R_2 R_3 R_5)$$

$$L_1 = c (R_2 R_3 R_4 / R_3 + R_2 R_4 R_5 / R_3 + R_2 R_3 R_5 / R_3)$$

$$\Rightarrow L_1 = c R_2 (R_4 + R_4 R_5 / R_3 + R_5)$$

$$L_1 = c R_2 (R_4 + R_5 + R_4 R_5 / R_3)$$

$$-\frac{j R_1 R_3}{\omega c} = -\frac{j R_2 R_4}{\omega c} ; R_1 R_3 = R_2 R_4$$

$$R_1 = R_2 R_4 / R_3$$

- This method is capable of precise measurement of inductances a wide range of values from a few μH to several Henries.

Advantages of Anderson Bridge:-

The following are the advantages of the Anderson's Bridge.

- 1.The balance point is easily obtained on the Anderson bridge as compared to Maxwell's inductance capacitance bridge.
2. The bridge uses fixed capacitor because of which accurate reading is obtained.
- 3.The bridge measures the accurate capacitances in terms of inductances.

Disadvantages of Anderson Bridge:-

The main disadvantages of Anderson's bridge are as follow.

- 1.The circuit has more arms which make it more complex as compared to Maxwell's bridge. The equation of the bridge is also more complex.
- 2.The bridge has an additional junction which arises the difficulty in shielding the bridge.

Because of the above-mentioned disadvantages, Maxwell's inductance capacitance bridge is used in the circuit.